


INTRODUCTION TO CURRENT ELECTRICITY

1. By recharging the accumulator. ✓ (03 marks)

Explan

The accumulator is connected to a d.c supply. ✓
The positive terminal of the accumulator is connected to the positive terminal of the electrical source and negative terminal to the negative terminal of the electrical source.

2.

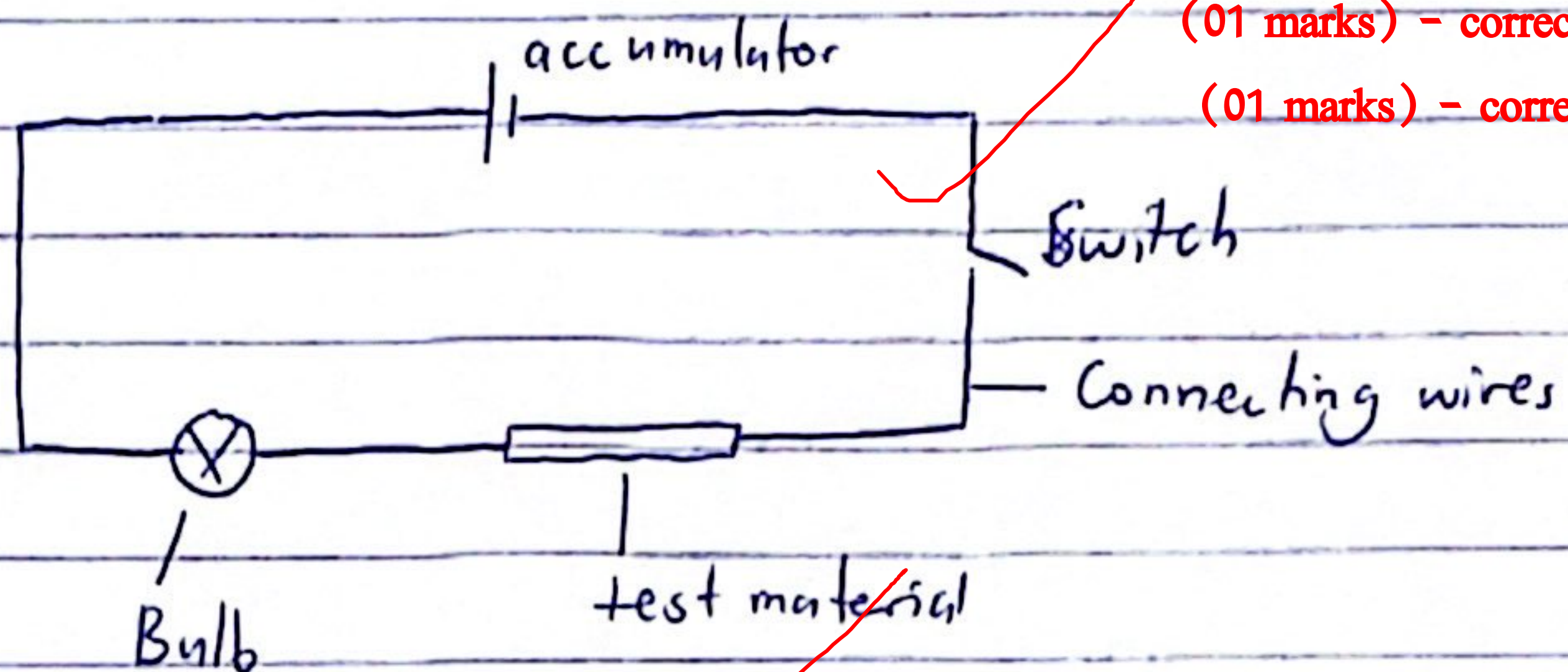

(01 marks) - correct illustration

(01 marks) - correct labelling

3. When the bulb lights, the material inserted in the circuit allows electric current to pass through it. ✓
the circuit becomes complete. ✓
Electric charges flow from the accumulator through the wires, bulb filament and the test material. (03 marks)

4. Conductors

- Copper wire ✓
- Iron nail
- Aluminium foil
- Graphite

(01 marks) - all correct

Insulators

- Plastic ruler ✓
- Rubber band
- Wooden stick
- Piece of cardboard.

(01 marks) - all correct